

AC Circuit MCQs: 101 to 105

**101 The inductive reactance is given by**

- ( a )  $\omega C$
- ( b )  $\pi f L$
- ( c )  $2\pi f L$
- ( d )  $L / 2\pi f$

Correct Answer ( c ):  $2\pi f L$

The inductive reactance is given by  $X_L = 2\pi f L$

**102 The voltage vector \_\_\_\_\_ current vector in the series RL circuit.**

- ( a ) Leads
- ( b ) Lags
- ( c ) Is in phase with
- ( d ) Any of the above

Correct Answer ( b ): Lags

The series RL circuit is inductive circuit due to presence of inductance L so it is lagging circuit.

**103 The true power in the series R - L circuit is given by**

- ( a )  $VI \times \text{Load factor}$
- ( b )  $VI \times \text{Power factor}$
- ( c )  $VI \times \text{Form factor}$
- ( d ) None of the above

Correct Answer ( b ):  $VI \times \text{Power factor}$

The true power or useful power is given by  $VI \times \text{Power factor}$  whereas the wattless component or reactive power is given by  $VI \times \sin \Phi$ .

**104 The cosine of angle between voltage vector and current vector is known as**

- ( a )Power factor
- ( b )Load factor
- ( c )Form factor
- ( d )Peak factor

Correct Answer ( a ): Power factor

The power factor is defined as the cosine of angle between voltage vector and current vector.

**105 The ratio of true power to the apparent power is known as**

- ( a )Power factor
- ( b )Load factor
- ( c )Form factor
- ( d )Peak factor

Correct Answer ( a ): Power factor

Power factor =  $VI \cos \Phi / VI$

= Active power / Apparent power

AC Circuit MCQs: 106 to 110

**106 The power factor is a ratio of**

- ( a ) $R / Z$
- ( b ) $X / Z$
- ( c ) $R^2 / Z$
- ( d ) $Y / Z$

Correct Answer ( a ):  $R / Z$

If R, X and Z are component of triangle where Z = impedance of circuit, X = reactance of circuit and R = Resistance of circuit

$\cos \Phi = R / Z$

**107 The active power is better known as**

- ( a )Idle component
- ( b )Wattless component
- ( c )Wattful component
- ( d )None of the above

Correct Answer ( c ): Wattful component

**108 Which of the following component is responsible for power factor?**

- ( a )VI
- ( b )VI Cos  $\Phi$
- ( c )VI Sin  $\Phi$
- ( d )VI tan  $\Phi$

Correct Answer ( c ): VI Sin  $\Phi$

The reactive power is responsible for power factor. If the reactive power increases, power factor decreases and vice versa. E.g.

Let  $\Phi = 0$  degree

$$\text{Active power} = VI \cos 0 = VI$$

$$\text{Reactive power} = VI \sin 0 = 0$$

Let  $\Phi = 45$  degree

$$\text{Active power} = VI \cos 45 = VI / \sqrt{2}$$

$$\text{Reactive power} = VI \sin 45 = VI / \sqrt{2}$$

Let  $\Phi = 90$  degree

$$\text{Active power} = VI \cos 90 = 0$$

$$\text{Reactive power} = VI \sin 45 = 1$$

From the above, as the reactive power increases, active power increases or power factor decreases considering product of VI remains constant.

**109 The reactive power is better known as**

- ( a )VI
- ( b )VI Cos  $\Phi$
- ( c )VI Sin  $\Phi$
- ( d )kVA

Correct Answer ( c ): VI Sin  $\Phi$

**110 The product of the RMS voltage and RMS current is known as**

- ( a )Reactive power
- ( b )Active power
- ( c )Apparent power
- ( d )Real power

Correct Answer ( c ): Apparent power

Active power = VI Cos  $\Phi$

Reactive power = VI Sin  $\Phi$

Apparent power =  $\sqrt{(\text{active power})^2 + (\text{Reactive power})^2} = VI$

AC Circuit MCQs: 111 to 115

**111 The power developed in the inductive reactance of the series R - L circuit is known as**

- ( a )Apparent power
- ( b )Active power
- ( c )Reactive power
- ( d )DC power

Correct Answer ( c ): Reactive power

**112 The power dissipated in the series R - L circuit is better known as**

- ( a )Active power

( b )Reactive power

( c )Apparent power

( d )Idle power

Correct Answer ( a ): Active power

**113 The reciprocal of the power factor is**

( a )Load factor

( b )Real factor

( c )P - factor

( d )Q factor

Correct Answer ( d ): Q factor

Power factor  $\cos \Phi = R/Z$

Reciprocal of power factor is known as quality factor  $Q = Z/R$

**114 The Q factor of the series R - L circuit is**

( a ) $X_L / R$

( b ) $Z / R$

( c ) $1 / R$

( d ) $L / R$

Correct Answer ( b ):  $Z / R$

The impedance of series RL circuit  $Z = R + j X_L$

Q factor of series RL / RC circuit is always  $Z/R$

**115 The current vector leads voltage vector in the series**

( a )R - L circuit

( b )L - C circuit

( c )R - C circuit

( d )R - L - C circuit

Correct Answer ( c ): R - C circuit

The current leads voltage vector in the series RC circuit whereas it lags in the series RL circuit.

AC Circuit MCQs: 116 to 120

**116 The power factor of the series R - C circuit is**

- ( a )Unity
- ( b )Lagging
- ( c )Leading
- ( d )Zero

Correct Answer ( c ): Leading

Due to capacitance of the circuit, power factor is leading

**117 The power factor of the series R - L - C circuit is**

- ( a )Unity
- ( b )Lagging
- ( c )Leading
- ( d )Any of the above

Correct Answer ( d ): Any of the above

Two parameter affects the power factor of series RLC circuit:  $X_L$  and  $X_C$

Inductive reactance =  $X_L$

Capacitive reactance =  $X_C$

If

$X_L > X_C$  = Inductive circuit, lagging power factor

$X_L < X_C$  = Capacitive circuit, leading power factor

$X_L = X_C$  = Resistive circuit, Unity, leading power factor

**118 The net reactance of the series R - L - C circuit is**

- ( a )R
- ( b ) $X_L + X_C$
- ( c ) $X_L - X_C$
- ( d ) $X_L - X_C$

Correct Answer ( c ):  $X_L \sim X_C$

Net reactance of series RLC circuit is  $X_L \sim X_C$

$X_L > X_C$  = Inductive circuit, lagging power factor

$X_L < X_C$  = Capacitive circuit, leading power factor

**119 The current leads voltage in the series R - L - C circuit when**

- ( a ) $X_L = X_C$
- ( b ) $X_L > X_C$
- ( c ) $X_C > X_L$
- ( d ) $R = 0$

Correct Answer ( c ):  $X_C > X_L$

Current leads voltage vector means capacitive circuit so  $X_C > X_L$

If current lags voltage vector, inductive circuit so  $X_L > X_C$

**120 The voltage leads current in the series R - L - C circuit when**

- ( a ) $Z = 0$
- ( b ) $X_L = X_C$
- ( c ) $X_C > X_L$
- ( d ) $X_L > X_C$

Correct Answer ( d ):  $X_L > X_C$

Voltage leads current, it means that current lagging therefore it is inductive circuit. In the inductive circuit,  $X_L > X_C$

Download AC Circuit MCQs PDF

[www.electrfunda.com](http://www.electrfunda.com)